

# Video DIGITISER

- ★ Resolution 312 x 255
- ★ 8-bit Luminance Resolution
- ★ Controller Board to detect Line & Synch Pulses Available

by Mark Brighton and  
Robert Kirsch

**A** Video Digitiser is a device which converts a video picture, such as the output of a video camera or V.C.R. (still frame) into digital words representing the luminance or brightness of coordinates (X, Y) within the picture. Thus, by sampling and converting all coordinates in turn, a stream of digital words representing the video picture may be sent to a host microcomputer and displayed on a graphics screen, or stored on disk or tape.

The resolution of the final computer picture will depend on the graphic capability of the host computer, up to the limits of the Digitiser.

In this case, the maximum vertical resolution of the Digitiser is the same as the number of complete lines in a video frame, i.e. 312 (although twice this number should be available if the interlace frame is also stored).


The horizontal resolution is 255 which is the possible number of sample points in one line scan, although some of these will be in non-valid picture area.

The resolution of the luminance samples is 8-bit for a standard video level,  $\approx 1$  volt of video. Most microcomputers will not be able to combine these resolutions in a graphic screen, and a compromise between (X, Y) resolution and luminance resolution will have to be made when programming.

## Circuit Description

In Figure 1, the video content of the incoming signal is stripped off by TR1 to leave composite sync, which is further split into frame sync by TR2/TR3 and line

12

 

sync by TR4/TR5. The line sync is externally wired to L.S.I. (Line Sync In) and controls the sample counter.

The sample counter (IC3,4) is preset by an incoming line sync pulse inverted by IC2b, a position byte having been set up on DP0-7 by an 8-bit output port from the host computer.

The line sync pulse also clocks flip-flop IC5 via OR gate IC6d, setting IC5 output high and enabling the oscillator IC1b via IC1c, which is used as a Schmitt Inverter.

This oscillator clocks the sample counter at a frequency determined by RV1/C4 ( $\approx 4$ MHz) and causes it to count down to zero and carry, disabling the oscillator by resetting IC5 via IC6d to prevent any further sample pulses during the present line.


The carry pulse is inverted by IC2c, and charges C9 which then discharges through R2, lengthening the pulse inverted by IC2a to operate the analogue switch IC8. This connects DC restored video from C25/D2 to the hold capacitor C8, which charges to the video voltage. The lengthened carry pulse is also

inverted by IC2f whose output goes to the 'Start of Conversion' input on the analogue to digital converter IC10. When the pulse ends, the analogue switch opens and the 'Held' video voltage is applied to IC10 via IC9, a high input impedance op-amp connected as a voltage follower, i.e. unity gain.

The End Of Conversion (EOC) output from IC10 goes low enabling the clock oscillator IC1d via an emitter follower TR6 and IC1a which is connected as a Schmitt Inverter. After the ninth cycle of the oscillator, the EOC output of IC10 goes high, disabling IC1d and indicating end of conversion. This signal is sent to the host computer, indicating that the output of the A/D converter is valid. The host computer reads and stores the data on P(DA) via an 'X' bit input port, where 'X' is the required number of luminance bits.

 IC7 is a voltage converter which produces a  $-5$  Volt supply for IC9 and IC10.





## Construction

Referring to the Parts List and PCB layout diagram (Figure 2), insert and solder veropins 1 to 6 from the underside of the board (Side 1) and fit Link 1 if termination of the video signal is required. Insert and solder in position all resistors, capacitors and diodes, taking note of polarity.

Insert and solder all IC sockets, transistors, BR1 and mount REG1 using the insulating washer and heatsink supplied, first smearing mating surfaces with heat transfer compound (not supplied).

Double check your work for short circuits, components in wrong places, etc. Five minutes careful examination of your work now may save much time and expense later.

Plug IC7 into its socket, ensuring correct orientation.

## Testing

Minimum system I/O requirement is one 8-bit output port and one 8-bit input port. This allows for up to 5 bits of luminance information, which should be

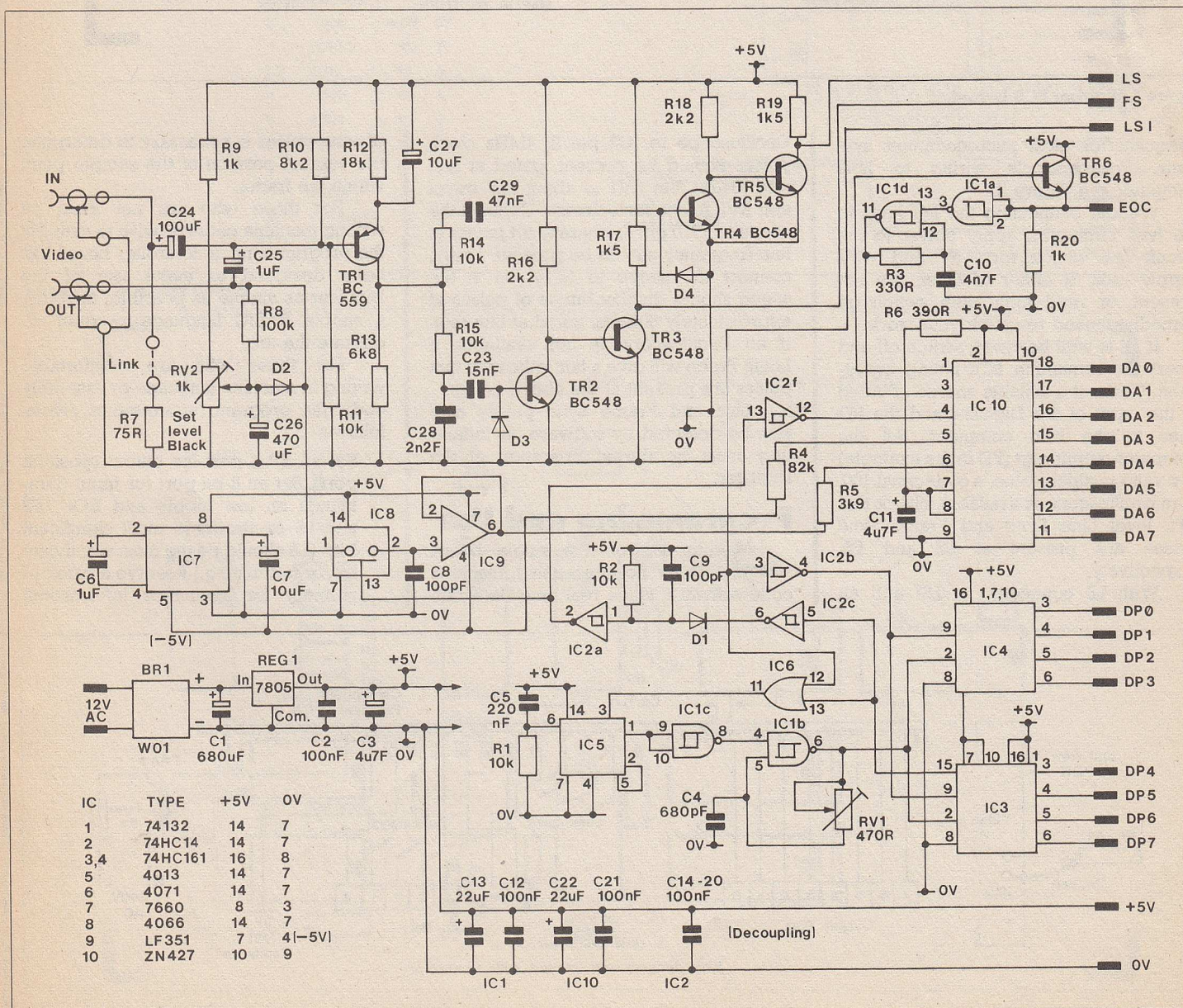


Figure 1. Digitiser Circuit  
December 1985 Maplin Magazine



 


Figure 2. Digitiser PCB Layout

adequate for most microcomputer systems. For example wiring to host computer see Figure 3.

Without connecting the I/O lines to the host computer, apply power to the circuit and check for +5V and -5V supply rails. If either of these are not present, or read high, then switch off immediately and re-check your work.

If all is well however, switch off and insert the remaining IC's noting orientation. Connect a suitable source of video to the input of the Digitiser and the I/O lines to the host computer. Set the computer output port (PD in the example) to a valid position value, e.g. decimal 100. If an oscilloscope is available, check that TTL level Line Sync and Frame Sync pulses are present at LS and FS, respectively.

With LS connected to LSI and an

Oscilloscope to IC3 pin 2, 4MHz clock pulses should be present, gated at line rate (64µs). Set RV1 to about half travel and RV2 fully anticlockwise. Connect the scope to IC10 pin 4, where short pulses at line frequency should be present. Lastly, connect the scope to IC10 pin 3; the scope should display bursts of pulses at approximately 600kHz, gated at line rate. If an Oscilloscope is not available, a Logic Probe will give a fair indication that pulses are present at the above points.

Line and Frame Sync pulses may also be detected by software, as indeed they must be during operation of the Digitiser.

### Programming and Use

Making use of this single board system is only possible using machine code software, since real time detection

of sync pulses is necessary to determine the vertical position of the sample point within the frame.

For those who are not keen on writing machine code, or wish to simplify the programming, a controller board has been designed to make use of the Digitiser as simple as possible, enabling a simple BASIC language program to operate the unit.

For those who are comfortable writing in machine language or assembly code, the program requirements are as follows:-

1. Set an 8-bit port for output (position port). Set an 8-bit port for input (luminance on low nibble and EOC, FS and LS on the three most significant bits. (LS should be the most significant bit for fast testing.) Reserve a block of memory for luminance information,

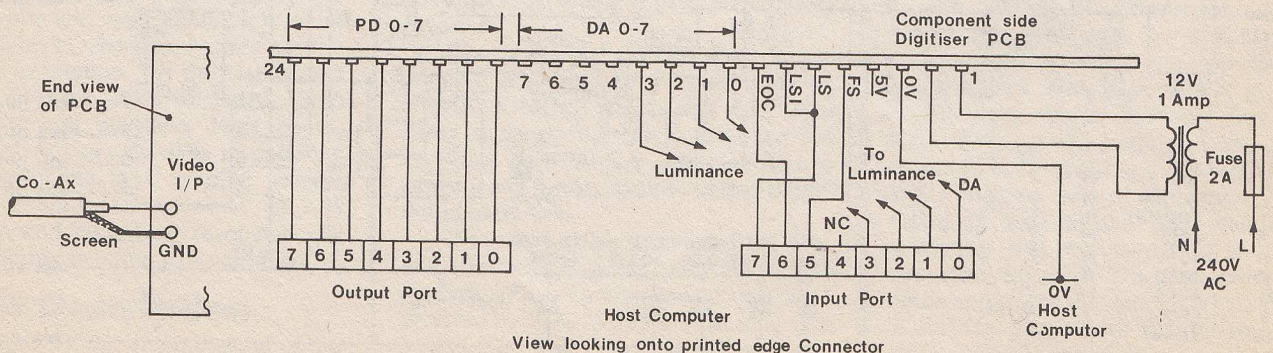


Figure 3. Board System Wiring



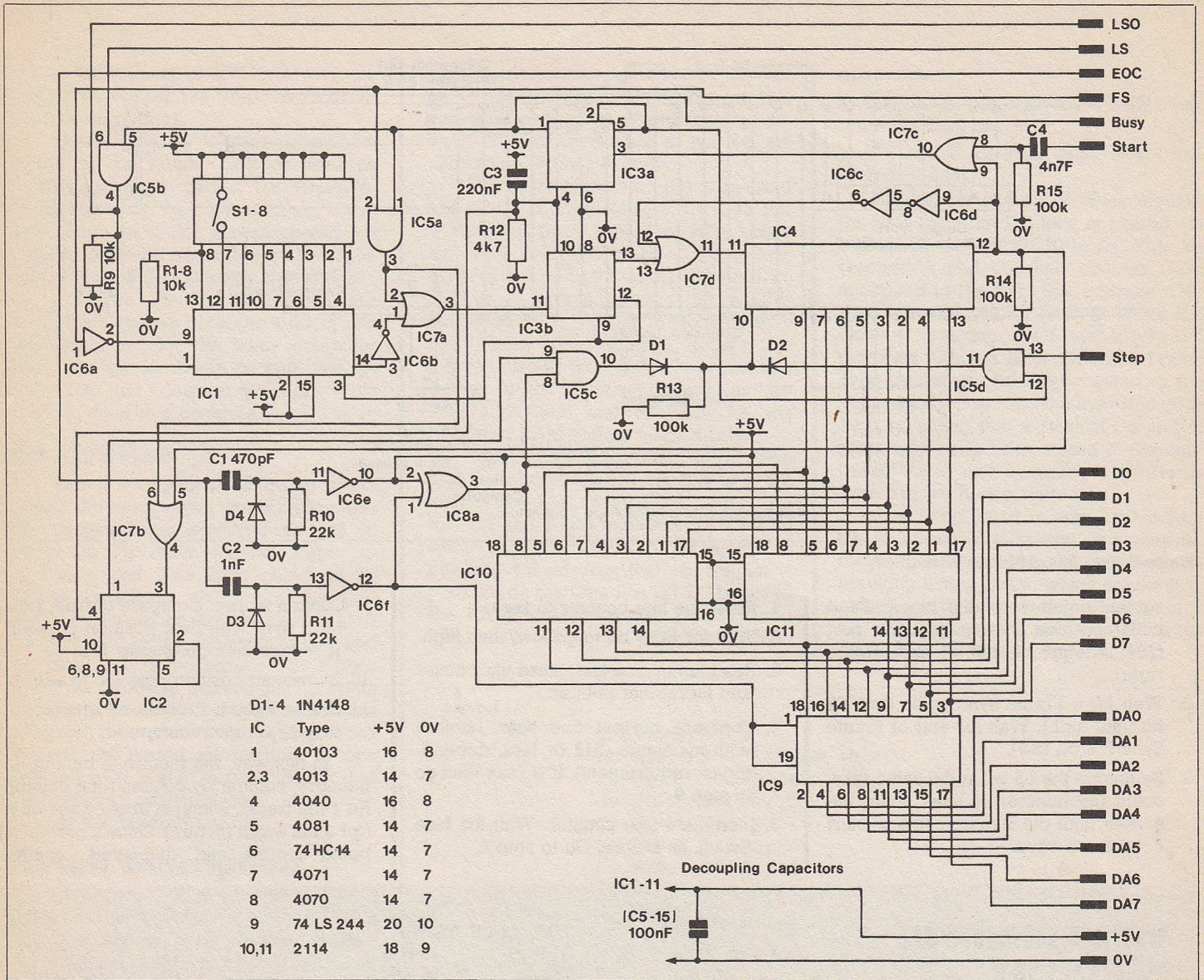


Figure 4. Controller Circuit

 


Figure 5. Controller PCB Layout  
 December 1985 Maplin Magazine



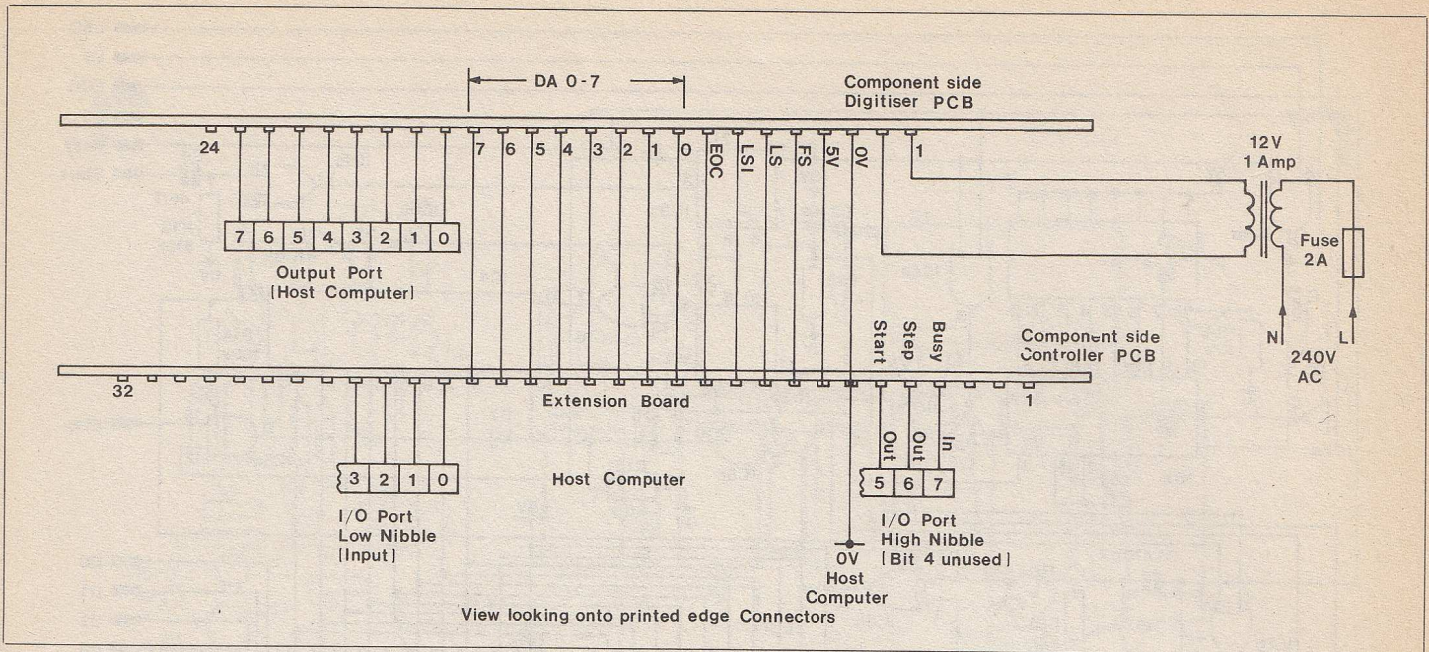


Figure 6. Two Board System Wiring

1. set up pointers to this block. Send initial position byte to position port (254 is extreme left, 0 is extreme right).
  2. Wait for a Frame Sync pulse (test FS bit until high). Wait for end of Frame Sync (FS bit low).
  3. By testing the LS bit in the same way, count the number of lines down the screen until the required line to start conversion occurs.
  4. Reset the line counter to zero.
  5. Wait for EOC bit to go low, then high.
  6. Read luminance bits, store via pointer and increment pointer.
  7. Compare current line scan number with maximum (312 or less, depending on requirement). If  $\geq$  max then go to step 9.
  8. Increment line counter. Wait for Line Synch. as before. Go to step 5.
  9. Column stored. Compare current position byte with final position number. If  $\geq$  max then go to step 11.
  10. Increment position port. Go to step 2.
  11. Frame stored. Process information to display on microcomputer.
- In this way, the picture is built up in memory, column by column (one column for each frame, 20ms) in about 5 seconds (for a full width picture). Once a picture is being stored and displayed, contin-

## VIDEO DIGITISER PARTS LIST

### RESISTORS: All 0.6W 1% Metal Film

R1,2,11,14,15	10k	5	(M10K)
R3	330R	1	(M330R)
R4	82k	1	(M82K)
R5	3k9	1	(M3K9)
R6	390R	1	(M390R)
R7	75R	1	(M75R)
R8	100k	1	(M100K)
R9,20	1k	2	(M1K)
R12	18k	1	(M18K)
R13	6k8	1	(M6K8)
R16,18	2k2	2	(M2K2)
R17,19	1k5	2	(M1K5)
R10	8k2	1	(M8K2)
RV1	470R Hor Sub-Min Preset	1	(WR54J)
RV2	1k Hor Sub-Min Preset	1	(WR55K)

### CAPACITORS

C1	680µF 40V Axial Electrolytic	1	(FB79L)
C2,12,14-21	100nF Minidisc	10	(YR75S)
C3	4µF 63V P.C. Electrolytic	1	(FF03D)
C4	680pF Ceramic	1	(WX66W)
C5	220nF Poly Layer	1	(WW45Y)
C6,25	1µF 100V P.C. Electrolytic	2	(FF01B)
C7,27	10µF 50V P.C. Electrolytic	2	(FF04E)
C8,9	100pF Ceramic	2	(WX66L)
C10	4nF Poly Layer	1	(WW26D)
C11	4µF 16V Tantalum	1	(WW64U)
C13,22	22µF 16V Tantalum	2	(WW72P)
C23	15nF Poly Layer	1	(WW31J)
C24	100µF 10V P.C. Electrolytic	1	(FF10L)
C26	470µF 16V P.C. Electrolytic	1	(FF15R)
C28	2nF Poly Layer	1	(WW24B)
C29	47nF Minidisc	1	(YR74R)

### SEMICONDUCTORS

D1-D4	1N4148	4	(OL80B)
TR1	BC859	1	(QQ18U)
TR2,3,4,5,6	BC548	5	(QB73Q)
BR1	W01	1	(QL38R)
REG1	µA7805UC	1	(QL31J)
IC1	74132	1	(WH03D)
IC2	74HC14	1	(UB10L)
IC3,4	74HC161	2	(UB41U)
IC5	4013BE	1	(QX07H)
IC6	4071BE	1	(OW43W)
IC7	7660	1	(YY75S)
IC8	4066BE	1	(QX23A)
IC9	LF351	1	(WQ30H)
IC10	ZN427	1	(UF40T)

### MISCELLANEOUS

Digitiser PCB	1	(GD02C)
Vaned Heatsink	1	(FL58N)
Kit (P) Plas	1	(WR23A)
DIL Socket 8-Pin	2	(BL17T)
DIL Socket 14-Pin	5	(BL18U)
DIL Socket 16-Pin	2	(BL19V)
DIL Socket 18-Pin	1	(HQ76H)
Connectector 124	1	(FL85G)
Edge Conn. End Bkt.	2	(YR58N)
Bolt 6BA x 1/2in.	1 Pkt	(BF06G)
Nut 6BA	1 Pkt	(BF18U)
Transformer 12V 1A	1	(WB25C)

A kit of parts is available for this project:  
**Order As LK95D (Digitiser Kit) Price £41.95**  
 The following item included in the above kit list is also available separately, but is not shown in the 1986 catalogue:  
**Digitiser PCB Order As GD02C Price £11.95**



ously, adjustment of RV1 will vary the aspect ratio to suit the graphics mode of the host computer.

The digitised pictures could be stored on an 'album' disk or used as backgrounds, for games for example. Some animation may be possible, if the host computer allows screen paging, by flipping between several stored images with slightly different subject positions.

However the stored images are used, this Digitiser provides a novel and interesting use for the home computer when the games begin to pall, and an answer to that recurrent question: 'What can you do with a computer?'

## Controller

This is an optional extension of the Video Digitiser, which greatly simplifies the programming required to use it. Using the Controller, software detection of Frame and Line Sync pulses is no longer necessary, this being handled solely by hardware. In operation, a start pulse is sent to the controller board and the busy line is monitored until it goes low. This indicates that a column of data has been stored which is read by the host computer, using the step input to scan through the stored information. A new position byte is sent to the Digitiser and the process repeated until the whole picture has been stored.

## Circuit Description

In Figure 4, upon receipt of a start pulse at CLK of IC3a via OR gate IC7c and C4/R15, a pulse length limiting network, the Q output of IC3a goes high, gating Line Sync pulses to LSO (Line Sync Out) which is connected to the sample pulse generating circuit on the Digitiser board. IC3a Q output also gates Frame Sync to IC3b via OR gate IC7a, causing IC3b Q output to go high upon receipt of the next Frame Sync pulse (start of picture). This holds line counter (IC4) reset via OR gate IC7d, while the Q output of IC3b enables counter IC1, a

presetable counter that counts a number of 'wasted' lines before carrying, i.e. sets vertical start position of digitised picture. Note, this number should not be set (Dipswitch) higher than 55.

The carry pulse from IC1 is inverted and clocks IC3b, resetting it, via IC7a. IC1 is disabled by Q output of IC3b going high and IC4 enabled by Q going low. IC2 was clocked by Frame Sync via IC7,5 and its Q output gates CHIP SELECT pulses from IC8 through to clock input of IC4. These CHIP SELECT pulses are derived from the end of conversion output of the Digitiser board, as are WRITE ENABLE and ENABLE for the RAM and RAM Buffer, respectively.

WRITE ENABLE comes from pulse shaping circuit C1/R10 via IC6 and the longer ENABLE pulse from C2/R11 via IC6. CS and E are exclusively OR'ed by IC8 to produce CS. Using this method to produce CS ensures that no conflict is possible on the Data Bus D0-D7 between the RAM and the Buffer (IC10/11 and IC9), since CS can only be low (active)

when either:-

- a)  $\overline{WE}$  and  $\overline{E}$  are both low. (Buffer has control of Bus) or,
- b)  $\overline{WE}$  and  $\overline{E}$  are both high. (RAM has control of Bus).

Under the control of these signals, the data from the Digitiser is passed via buffer IC9 to RAM (IC10/11 for eight bit resolution) and the line counter (IC4) advanced to the next line address. This process continues for each line until IC4 carries, resetting itself via IC6/7 and resetting IC3a via IC7c. Line and Frame Sync pulses are no longer gated to the counters/flip-flops and the busy line goes low, indicating that a vertical column of screen data has been stored in the controller RAM, and is ready to be transferred to the host computer.

The 'step' input is now enabled by the Q output of IC3a and data may be transferred by reading the Data Bus and applying a step pulse, which clocks IC4, stepping it to the next line address, until all data has been read ( $\leq 256$  lines depending on system requirement).

### Listing 1.

```

5 GRAPHICS 9
10 REM .* SET UP PORTS *
20 POKE 54019,56
30 POKE 54017,255
40 POKE 54019,60
50 POKE 54018,56
60 POKE 54016,112
70 POKE 54018,60
80 C=0
100 PA=54016:PB=54017
200 POKE PB,230
250 POKE PA,64:POKE PA,0
300 IF PEEK(PA)/128>=1 THEN GOTO 300
400 FOR X=0 TO 191:LUM=PEEK(PA)
410 GOSUB 2000:POKE PA,32
420 POKE PA,0:NEXT X
430 C=C+1:POKE PB,230-C
500 GOTO 250
2000 IF C=80 THEN GOTO 2000
2010 COLOR LUM:PLOT C,X:RETURN

```

## DIGITISER CONTROLLER PARTS LIST

RESISTORS: All 0.6W 1% Metal Film

R1-9	10k	9	(M10K)
R10,11	22k	2	(M22K)
R12	4k7	1	(M4K7)
R13,14,15	100k	3	(M100K)

### CAPACITORS

C1	470pF Ceramic	1	(WX64U)
C2	1nF Poly Layer	1	(WW22Y)
C3	220nF Poly Layer	1	(WW45Y)
C4	4n7F Poly Layer	1	(WW26D)
C5-15	100nF Minidisc	11	(YR78S)

### SEMICONDUCTORS

D1-4	1N4148	4	(QL80B)
IC1	40103BE	1	(QW61R)
IC2,3	4013BE	2	(QX07H)
IC4	4040BE	1	(QW27E)
IC5	4081BE	1	(QW48C)

IC6	74HC14	1	(UB10L)
IC7	4071BE	1	(QW43W)
IC8	4070BE	1	(QX26D)
IC9	74LS244	1	(QO66L)
IC10,11	2114	2	(QW12N)

### MISCELLANEOUS

S1	Digitiser Controller PCB	1	(GD03D)
	DIL Switch SPST (Octal)	1	(XX27E)
	Connector 132	1	(FL86T)
	Edge Conn. End Bkt.	2	(YR68N)
	DIL Socket 18-Pin	2	(HQ76H)
	DIL Socket 20-Pin	1	(HQ77T)
	DIL Socket 14-Pin	6	(BL18U)
	DIL Socket 16-Pin	3	(BL19V)

A kit of parts is available for this project:

Order As LK96E (Digitiser Controller Kit) Price £29.95

The following item included in the above kit list is also available separately, but is not shown in the 1986 catalogue: Digitiser Controller PCB Order As GD03D Price £11.95




## Construction

Locate and solder all resistors, capacitors and diodes, noting polarities. Fit and solder Dipswitch and all IC sockets, locating Dipswitch with the writing on its side facing the edge of the board, and the polarity notches of the IC sockets matching the square block marked on each IC legend. See Figure 5. Carefully insert all IC's in their respective positions, taking note of correct orientation. Wire the edge connector as shown in Figure 6, referring to your computer manual or instructions for your I/O port, where applicable. Keep all wiring between the boards and the computer as short as possible to avoid corruption of data. Take care to check all joints/connections for short circuits, dry joints, etc.
 
## Testing

Plug both boards into their edge connectors and apply power. Check the



5V supply using a multimeter. IC3 pins 1 and 13, IC2 pin 1 should all be low (<1V), relative to 0V. All being well, switch off and connect the circuits to the host computer and video source as shown in Figure 6.

## Programming

Listing 1 shows a BASIC language program to operate the Digitiser. The

addresses given relate to the port addresses of the Atari 400/800 computers. A BASIC program will take several minutes to complete the screen display, but has the advantage of being very quick and easy to write. For those who desire faster operation, a machine code program will be required. An example (Listing 2) is provided in 6502 assembly language, again for the Atari 400/800 computers, although no explanation of this program will be included here, this being beyond the scope of the present article.

Throughout this article, it has been assumed that the reader has a basic understanding of the construction of a video signal. For those who wish to gain some knowledge on the subject, the following book is recommended:

Questions and Answers on Video by Steve Money, available from Maplin (Stock Code WG77J).

Listing 2.

```

10  *=$7000
20  PORTA=$D300
30  PORTB=$D301
40  PACTL=$D302
50  PBCTL=$D303
60  NMIEN=$D40E
70  IRQEN=$D20E
80  POKMSK=$0010
90  DMACTL=$D400
0100 SDMCTL=$022F
0110 SAVMC=$0058
0120 MASK=$06F9
0130 LINES=$06FA
0140 POSIT=$06FB
0150 SCNCOL=$06FC
0160 OFFSET=$00D4
0170 FINCOL=$06FE
0180          PLA
0190 INIT      LDA  #$00
0200          STA  LINES
0210          LDA  #240
0220          STA  POSIT
0230          LDA  SAVMC
0240          STA  SCNCOL
0250          LDA  SAVMC+1
0260          STA  SCNCOL+1
0270          CLC
0280          CLD
0290          TAX
0300          LDA  SCNCOL
0310          ADC  #40
0320          STA  FINCOL
0330          BCC  NOINT
0340          INX
0350 NOINT     STX  FINCOL+1
0360          LDA  #$38
0370          STA  PBCTL
0380          STA  PACTL
0390          LDA  #96
0400          STA  PORTA
0410          LDA  #$FF
0420          STA  PORTB
0430          LDA  #$3C
0440          STA  PBCTL
0450          STA  PACTL
0460 START     LDA  SCNCOL
0470          STA  OFFSET
0480          LDA  SCNCOL+1
0490          STA  OFFSET+1
0500          LDA  POSIT
0510          STA  PORTB
0520 TOG      LDA  #64
0530          STA  PORTA
0540          JSR  DELAY
0580          LDA  #0
0590          STA  PORTA
0600 HI       BIT  PORTA
0610          BMI  HI
0620 GETLUM   LDX  PORTA
0630          LDA  POSIT
0640          LSR  A
0645          LSR  A
0650          BCC  MULT
0660          TXA
0662          LDX  #240
0664          STX  MASK
0670          AND  #$0F
0680          JMP  STORE
0690 MULT     TXA
0692          LDX  #15
0694          STX  MASK
0700          ASL  A
0710          ASL  A
0720          ASL  A
0730          ASL  A
0740 STORE    LDY  #$00
0750          ORA  (OFFSET),Y
0760          STA  (OFFSET),Y
0762          LDY  #40
0764          LDA  (OFFSET),Y
0765          AND  MASK
0766          STA  (OFFSET),Y
0770 NEWROW  CLC
0780          CLD
0790          LDA  OFFSET
0800          ADC  #40
0810          STA  OFFSET
0820          BCC  LNCHK
0830          CLC
0840          INC  OFFSET+1
0850 LNCHK   INC  LINES
0860          LDA  LINES
0870          CMP  #191
0880          BCC  STEP
0890          LDA  #$00
0900          STA  LINES
0910 ODD     LDA  POSIT
0920          LSR  A
0925          LSR  A
0930          BCC  PICFIN
0940          CLC
0950          LDA  SCNCOL
0960          ADC  #$01
0970          STA  SCNCOL
0980          BCC  PICFIN
0990          INC  SCNCOL+1
1000 PICFIN   DEC  POSIT
1005          DEC  POSIT
1010          LDA  SCNCOL
1020          CMP  FINCOL
1030          BCC  NEWCOL
1040          LDA  SCNCOL+1
1050          CMP  FINCOL+1
1060          BCC  NEWCOL
1070 FIN      RTS
1080 STEP     LDA  #32
1090          STA  PORTA
1100          JSR  DELAY
1150          LDA  #0
1160          STA  PORTA
1170          JMP  GETLUM
1180 NEWPIC   LDA  #$16
1190          STA  POSIT
1200          LDA  SAVMC+1
1210          STA  SCNCOL+1
1220          LDA  SAVMC
1230          CLC
1240          ADC  #40
1250          STA  SCNCOL
1260          BCC  NEWCOL
1270          INC  SCNCOL+1
1280 NEWCOL   JMP  START
1290 DIS      LDA  #$00
1300          STA  IRQEN
1310          STA  POKMSK
1320          STA  NMIEN
1330          STA  DMACTL
1340          STA  SDMCTL
1350          RTS
1360 ENA      LDA  #$C0
1370          STA  IRQEN
1380          STA  POKMSK
1390          STA  NMIEN
1400          LDA  #34
1410          STA  DMACTL
1420          STA  SDMCTL
1430          RTS
1440 DELAY    LDX  #30
1450 DOWN     DEX
1460          BNE  DOWN
1470          RTS

```