

Australia \$1.75 New Zealand \$1.95 Malaysia \$4.96

PRACTICAL

MAY 1985 - £1.00

ELECTRONICS

ROBOTICS · MICROS · ELECTRONICS · INTERFACING



**AMSTRAD
Synthesiser
Interface**

Cylinder Thermostat

Stereo Noise Gate & VCA

Electronics at the BBC

CONSTRUCTIONAL PROJECTS

AMSTRAD SYNTHESISER INTERFACE by R. A. Penfold	10
1000 note, 5 octave sequencer—computer project	
STEREO NOISE GATE & VCA by John M. H. Becker	14
Reduces noise for musicians and home studio recording	
REMOTE SENSING THERMOMETER by Tom Gaskell BA(Hons) CEng MIEE	22
A 3½ digit electronic thermometer	
TELEPRINTER INTERFACE by B. Drake	26
Low cost letter quality prints from your computer	
CYLINDER THERMOSTAT by Mark Stuart	38
Enables economic use of hot water system	
RUGBY CONTROLLED CLOCK—Part 2 by Stephen Ibbs	53
Construction and setting up procedures	

GENERAL FEATURES



SEMICONDUCTOR CIRCUITS by Tom Gaskell BA(Hons) CEng MIEE	19
Temperature sensor (LM35)	
SPACEWATCH by Dr. Patrick Moore OBE	24
ELECTRONICS AT THE BBC by Chris Kelly	32
Inside the VAX 11/750 and the Quantel 7001 (Paintbox)	
BBC MICRO FORUM by D. Whitfield MA MSc CEng MIEE	44
We pop a numerical keypad into the cauldron	
BBC MICRO PRINTER SOFTWARE by Michael Tooley BA & David Whitfield MA MSc CEng MIEE	46
We look at two dedicated printer ROMs	

NEWS & COMMENT

EDITORIAL	7	NEXT MONTH	37	LEADING EDGE	58
NEWS & MARKET PLACE	8	BAZAAR	49	P.C.B. SERVICE	59
		INDUSTRY NOTEBOOK	50		



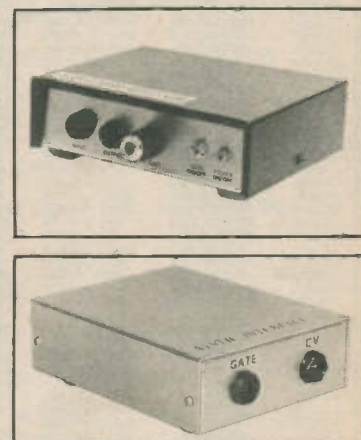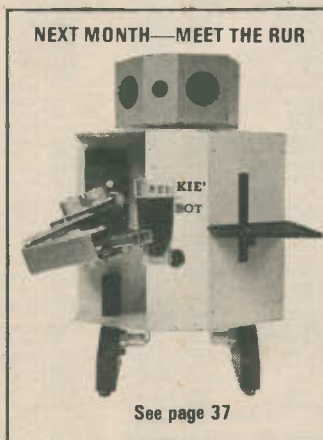This month's cover shows details of a probe card in use at Motorola's East Kilbride facility.



OUR JUNE ISSUE WILL BE ON SALE FRIDAY, MAY 3rd, 1985 (see page 37)

© IPC Magazines Limited 1985. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

AMSTRAD SYNTHESISER INTERFACE

R. A. PENFOLD



THE Amstrad CPC464 computer is a highly versatile machine which is well suited to many applications, including those associated with user add-ons. The interface which is described in this article, together with the correct software, enables the CPC464 to be utilized as a sequencer for a synthesiser which has the standard five volt gate/trigger pulse input and one volt per octave control voltage input. The note is programmable over more than five octaves (including all semitones), and the gate time, plus note duration are also programmable.

With its genuine 64K of RAM a large number of notes can be accommodated. In fact the program enables up to one thousand notes to be entered, and with a slight modification it could probably be made to take sequences several times longer than this. The program includes editing facilities, plus the ability to save sequences on tape and reload them when required.

SYSTEM OPERATION

Driving the gate or trigger input of most synthesisers is perfectly straightforward since all that is needed is a signal at standard TTL levels. A single bit digital output is therefore all that is required to drive this input. Driving the control voltage input is also fairly straightforward for a synthesiser which has standard one volt per octave (logarithmic) input.

With this type of synthesiser the control voltage from the keyboard is provided by a potential divider which has a series of equal value resistors. It thus provides a series of output voltages with an equal step size from one note to the next. It is quite easy to simulate this with a computer, and all that is required is a normal (linear) digital to analogue converter. With this type of converter, if writing '1' to the circuit gave an output voltage of (say) 10 millivolts, then '2' would give 20 millivolts, '3' would give 30 millivolts, and so on. The keyboard of a synthesiser gives increments of about 83 millivolts, and it is just a matter of scaling the output of the digital to analogue converter to precisely match this.

Note that some older synthesisers have a linear control voltage characteristic which, paradoxically, has a non-equal increment from one note to the next, but a linear relationship between the control voltage and the output frequency. Instruments of this type cannot be used with the interface featured in this article, and can not easily be interfaced to a computer.

The block diagram of Fig. 1 shows the general arrangement used in this interface. An address decoder is used to activate a single bit data latch when data is written to a suitable address, and this latch provides the gate or trigger

pulse signal. This output can be placed high or low, as desired, under program control. The address decoder also activates a six bit data latch which is used to drive the digital to analogue converter. The converter is in fact an ordinary eight bit type, but in this application only six bits are normally used as this is sufficient to give a range of 63 notes, which is about the limit for most synthesisers. The two least significant inputs of the converter are simply tied to the negative supply rail.

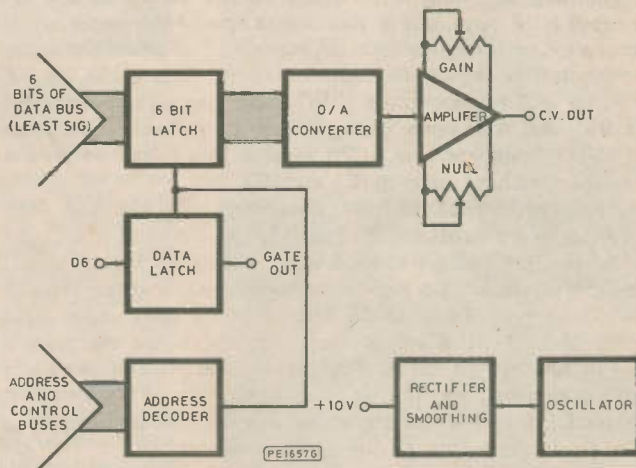


Fig. 1. Block diagram of the Amstrad Sequencer

The converter has an output that increments in units of nominally 10 millivolts, but as the two least significant bits are not used here this is boosted to 40 millivolts. This is not sufficient to drive the control voltage input of a synthesiser, and an amplifier is used to boost the output voltage by a factor of about two times.

A gain control enables the output voltage increment to be trimmed to exactly the correct figure. An offset null control enables any d.c. offsets in the system to be trimmed out so that good pitch accuracy is obtained at the low frequency end of the range.

The circuit is powered from the five volts output of the CPC464, and this is the only supply output which the machine provides. This is inadequate to drive the amplifier stage which must provide a maximum output voltage of just over five volts. This problem is overcome by rectifying and smoothing the output of an oscillator to produce a supply potential of about ten volts for the amplifier stage.

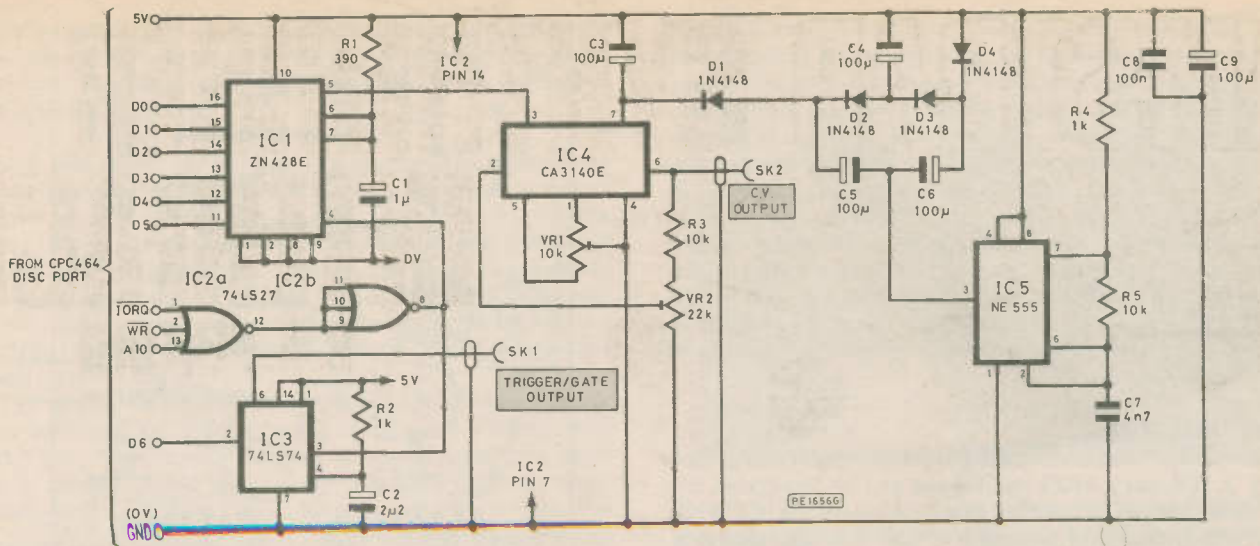


Fig. 2. Complete circuit diagram of the Amstrad Sequencer

CIRCUIT OPERATION

The full circuit diagram of the interface appears in Fig. 2. The unit connects to the floppy disc port of the computer which is really a general purpose port which makes available the full address, data, and control buses of the computer, as well as a number of other useful lines.

Address decoding is provided by IC2 which is a triple 3-input NOR gate, but in this circuit one of the gates is left unused, and the three inputs of one of the other gates are connected together so that this gate acts as a simple inverter. IC2a decodes the $\overline{\text{TORQ}}$ (input/output request), $\overline{\text{WR}}$ (write), and A10 lines, giving a high output when all three of these lines are low. IC2b inverts this signal to give a negative latching pulse to IC1 and IC3.

This method of address decoding may seem a little strange by conventional Z80 standards, with just one of the address lines being decoded with the relevant control bus lines, and one of the eight most significant address lines at that. However, the CPC464 does not have the conventional form of Z80 input/output mapping where the eight least significant lines of the address bus are decoded to give up to 256 addresses, and the eight most significant lines are left unused. Instead, input/output circuits are activated by taking the appropriate one of the eight most significant address lines low, while the eight least significant address lines are available for use if an input output device requires several addresses. This is similar although not identical to the system used in the Sinclair Spectrum computer.

Address line A10 is available for use with external add-ons, and it is therefore this line going low that is used to activate the sequencer interface. Of course, with only one address line being decoded there are numerous addresses that can be used to operate the interface, but in practice it is advisable to only use &F800 as with the only exception of A10 this leaves all the address lines high and will not produce spurious operations of internal circuits of the computer.

IC3 is a dual D-type flip-flop, but only one section is utilized here; it is used as a data latch with the latching pulse from the decoder circuit applied to the "clock pulse" input. The gate/trigger pulse is obtained from the $\overline{\text{Q}}$ output of the flip/flop.

The digital to analogue converter, IC1, is a Ferranti ZN428E. This is a conventional type having an integral 2.55V precision voltage source, eight electronic switches, and an R-2R resistor network. The voltage reference re-

quires discrete load resistor R1 and decoupling capacitor C1. The output from this stage is coupled to the input of an operational amplifier (IC4) which is used as a non-inverting amplifier. R3 and VR2 form the negative feedback network which set the closed loop voltage gain of the circuit, and VR2 is adjusted to give the correct level of voltage gain. VR1 is the offset null control for IC4.

COMPONENTS ...

Resistors

R1	390
R2,R4	1k (2 off)
R3,R5	10k (2 off)
All fixed resistors are 0.25W 5% carbon	

Potentiometers

VR1	10k 0.1W horizontal preset
VR2	22k 0.1W horizontal preset

Capacitors

C1	1 μ 63V radial elect
C2	2 μ 2 63V radial elect
C3-C6, C9	100 μ 10V radial elect (5 off)
C7	4n7 carbonate
C8	100n ceramic

Semiconductors

D1-D4	1N4148 (4 off)
IC1	ZN428E
IC2	74LS27
IC3	74LS74
IC4	CA3140E
IC5	NE555

Constructor's Note

A complete listing of the sequencer program is available for £1 inc. P&P from our editorial offices.

Miscellaneous

SK1, SK2 standard jack sockets (2 off)
 Printed circuit board PE 505-01
 Case 133 x 102 x 38mm
 2 x 25 way 0.1 inch pitch edge connector
 16 pin d.i.l. i.c. holder
 14 pin d.i.l. i.c. holders (2 off)
 8 pin d.i.l. i.c. holders (2 off)
 Ribbon cable, wire, connecting leads, etc.

IC4 is a CA3140E, a device which has a Class A output stage that enables output voltages right down to the 0V rail to be produced. This obviates the need for a negative supply rail. IC5 is a 555 timer device which operates in the standard astable mode. This is the oscillator which is used to provide the boosted positive supply for IC4. Its output is rectified and smoothed by D3, D4, and C6, and also by D1, D2, and C3. The resultant positive outputs are effectively connected in series together with the 5V supply so as to give a voltage tripling action. However, in practice losses through the diodes and the output stage of IC5 result in a loaded supply potential of only about 10V or so, but this is still more than adequate to permit IC4 to provide a peak output voltage of about five to six volts.

CONSTRUCTION

A suitable printed circuit design for this project is provided in Fig. 3. IC4 has a MOS input stage and an integrated circuit holder should be used for this component. As IC1 is not one of the cheapest of devices it is also advisable to use a socket for this component. Be careful to fit this device the right way round—it has the opposite orientation to the other integrated circuits. Fit Veropins at the points where the board will be connected to SK1 and SK2. Do not overlook the two link wires.

The board is connected to the floppy disc port of the computer by way of a piece of 13 way ribbon cable about 0.5 to 1 metre long and terminated in a 2 by 25 way 0.1 inch pitch female edge connector. A connector having a suitable polarising key is unlikely to be available, and care to fit the connector the right way round must be taken. It is advisable to clearly mark the top and bottom edges of the connector as such, or with a little ingenuity it might be possible to add a polarising key to the connector. Fig. 4 gives connection details for the edge connector.

An aluminium box having approximate outside dimensions of 133 by 102 by 38mm is used as the housing for the prototype, but any case of about this size should be satisfactory. SK1 and SK2 are standard jack sockets which match the connectors used on the vast majority of synthesisers, and they are mounted on the front panel.

The printed circuit board is mounted on any convenient area of the base panel of the case using 6BA or M3 fixings. If the case is a metal type it is obviously essential to use spacers to prevent the connections on the underside of the board from being short circuited through the case, and even if a non-metal case is used it is still advantageous to use spacers. This avoids any distortion of the board and possible damage when the mounting nuts are tightened.

Some means of taking the ribbon cable through the case must be found, and it may be possible to simply take it through the small gap between the top and base sections of the case. If this is not possible a suitable slit must be cut or filed in the rear panel of the case. To complete the unit the connections from the printed circuit board to SK1 and SK2 are added.

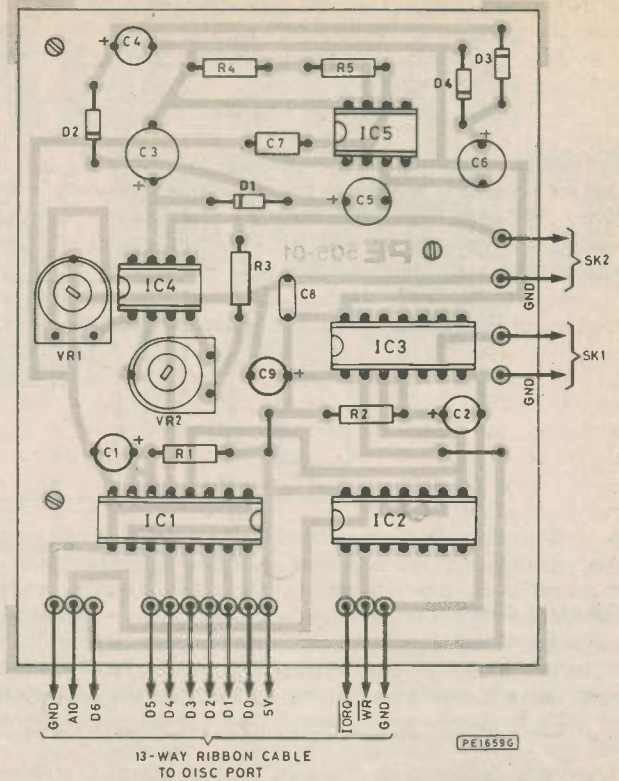


Fig. 3. P.c.b. design and component layout of the Amstrad Sequencer

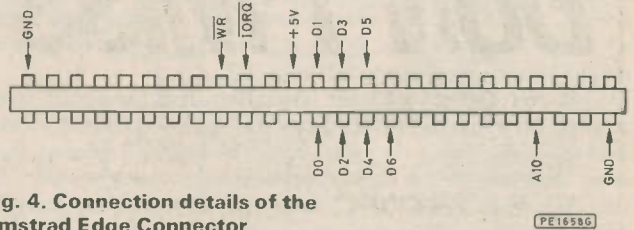


Fig. 4. Connection details of the Amstrad Edge Connector

ADJUSTMENT AND USE

Start with VR1 and VR2 at a roughly central setting. Connect the unit to the computer prior to switching on. The computer should display the usual ready message etc.—switch off at once and recheck the wiring if it does not. As a quick check of the unit the command:—

OUT &F800,0

should set the gate/trigger output high and the control voltage output at virtually zero. The command:—


OUT &F800,127

should set the gate/trigger output low, and the control voltage output at something in the region of 5V.

In order to set VR1 and VR2 at the correct settings, first set the control voltage output to give the lowest note using the command:—

OUT &F800,1

When using the interface remember that a value of '1' gives the lowest note, and the a value of '0' is not used as a note value. Connect SK1 and SK2 to the appropriate inputs of the synthesiser using standard jack leads. With most synthesisers it is necessary to have one or more of the controls in the right position before the external inputs will function properly, and the manual should give details of the correct control settings if you are in any doubt about this point.

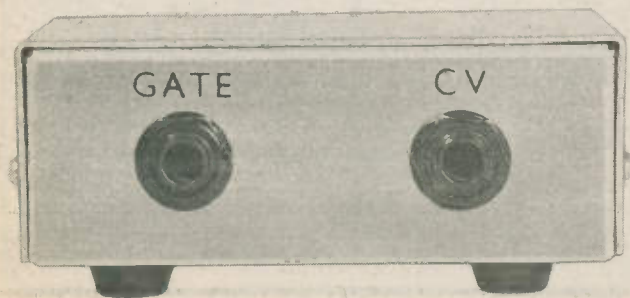


By adjusting VR1 it should be possible to vary the note from the synthesiser slightly. Adjust VR1 to obtain the same note that is produced by the lowest key of the keyboard. Using the command:—

OUT &F800,25

should give a note two octaves higher than the lowest note of the keyboard, and VR2 is adjusted to give precisely the correct note. It is advisable to repeat this procedure a few times until exactly the right note is obtained with both note values. The unit should then track perfectly at intermediate notes, and even if the keyboard only provides the usual two or two and a half octave range, most synthesisers are capable of producing the full five octave range using an external control voltage.

The suggested sequencer program enables note pitches, gate durations, and total note durations to be programmed, and it has other features such as automatic looping or playing a sequence just once. Gate and total note duration values are in 300ths of a second incidentally. As the program is menu driven and is largely self explanatory in use no further description is really needed here. For those who wish to design their own software the basic sequence is for the note value to be written to address &F800 using an OUT instruction, and this automatically sets the gate/trigger output high.

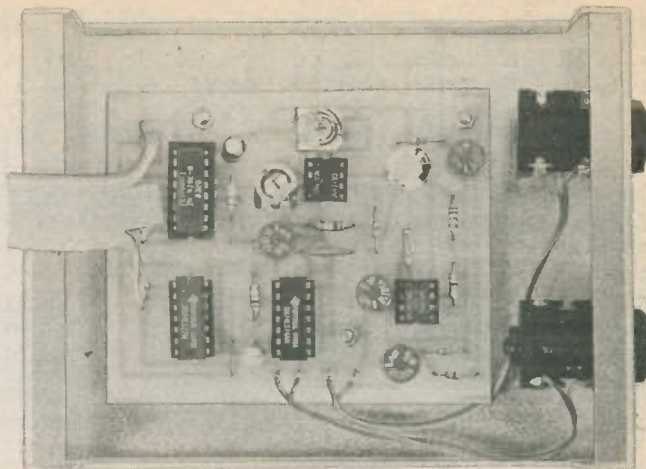To terminate the gate/trigger pulse a value of 64 plus the note value is written to address &F800 using an OUT in-



struction. The next note value is then written to &F800 after the appropriate time has elapsed. BASIC is normally fast enough for an application of this type, especially one of the faster versions such as the Locomotive BASIC used in the CPC464. However, if machine code is used to control the interface remember that output instructions which use the B register to provide the upper eight bits of the address bus must be used, since the CPC464 uses sixteen bit and not eight bit input/output addresses. ★

DON'T MISS A VITAL COPY!

Ever been in the middle of a project only to find the next issue sold out?
An annual subscription to **PRACTICAL ELECTRONICS** solves the problem.

Wherever you live you'll receive a copy regularly each month. It's the quick, practical way to solve delivery problems.

SUBSCRIPTION RATES

U.K. £13.00
Overseas £15.00

**COMPLETE
AND POST
THIS
ORDER FORM
TODAY!**

PRACTICAL

ELECTRONICS

SUBSCRIPTION ORDER FORM

Annual Subscription Rates	
U.K.	£13.00
Overseas	£15.00
(Students: deduct £1 and quote Student number)	

Complete this form and post it, with payment or credit card authorisation to:
Practical Electronics
Subscription Dept.
Oakfield House,
35 Perrymount Road,
Haywards Heath,
West Sussex RH16 3DH

POST COPIES TO

NAME _____

ADDRESS _____

POST CODE _____

I enclose my cheque/PO payable to IPC Magazines Ltd. for £ _____
Charge my credit card A/C at quoted rate

Card valid from _____ to _____

Signature _____


25

PRACTICAL ELECTRONICS PRINTED CIRCUIT BOARD SERVICE

Printed circuit boards for certain PE constructional projects are now available from the PE PCB Service, see list. They are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for overseas airmail. Remittances should be sent to: **PE PCB Service, Practical Electronics Editorial Offices, Westover House, West Quay Road, Poole, Dorset BH15 1JG.** Cheques should be crossed and made payable to IPC Magazines Ltd.

Please note that when ordering it is important to give project title, order code and the quantity. Please print name and address in Block Caps. Do not send any other correspondence with your order.

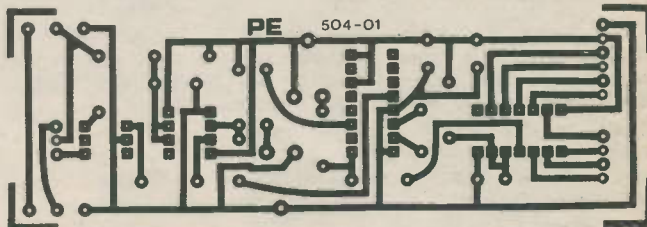Readers are advised to check with prices appearing in the current issue before ordering.



NOTE: Please allow 28 days for delivery. We can only supply boards listed here.

PROJECT TITLE	Order Code	Cost
FEB '81		
Slave Light Dimmer	102-01	£1.88
MAR '81		
27/28MHz Converter	103-01	£1.79
Microphone Mixer	103-02	£1.83
Period Power Tester	103-03	£2.25
APRIL '81		
Speech Processor	104-01	£1.55
Mini Drill	104-02	£1.50
MAY '81		
Digisounder	105-01	£6.65
Thermometer	105-02	£1.49
JUNE '81		
pH Meter	106-01	£2.06
SEPT '81		
Horologicum	109-01	£3.16
"	109-02	£3.11
"	109-03	£2.97
Analogue Frequency Meter	109-04	£2.87
Ignition System	109-05	£2.47
"	109-06	£2.28
APRIL '82		
Med. Resolution Equaliser (UK 101)	204-01	£1.73
Enlarger Timer	204-02	£4.02
AUG '82		
Automatic Photographer	208-01	£1.94
Home Alarm	208-02	£3.21
JAN '83		
Audio Booster	301-01	£3.32
FEB '83		
Radio Booster	302-02	£1.80
MAR '83		
Into the Real World	303-01	£3.99
Accessory PSU	303-02	£1.35
4½ Digit Frequency Meter	303-03	£3.69
JUNE '83		
Program Conditioner	306-01	£2.30
SEPT '83		
Guitar Active Tone Control	309-01	£2.27
Ground Communication System	309-02	£2.13
"	309-03	£2.31
DEC '83		
Expanding the Vic 20	312-01	£5.18
FEB '84		
Temp. Controller	402-04	£1.85
"	402-05	£2.61
MAR '84		
Spectrum Autosave	403-01	£1.83

PROJECT TITLE	Order Code	Cost
MAY '84		
Sustain Unit	405-02	£2.82
Audio Signal Generator	405-03	£4.28
"	405-04	£2.51
JULY '84		
EPROM Duplicator	407-02	£3.74
Alarm System	407-03	£3.19
Oscilloscope Calibrator	407-04	£4.23
AUG '84		
Comm. 64 RS232C Interface	408-01	£3.02
Field Measurement	408-02	£3.19
"	408-03	£2.76
Simple Logic Analyser	408-05	£2.93
SEPT '84		
Parallel to Serial Converter	409-01	£2.92
Through the Mains Controller	409-02	£2.88
"	409-03	£2.71
OCT '84		
Logic Probe	410-01	£1.90
NOV '84		
Computer DFM Adaptor	411-01	£2.76
DEC '84		
Ni-Cad Charger	412-01	£2.40
JAN '85		
Outrider Car Computer (Set of 2 boards)	501-01/2	£9.10
FEB '85		
Modular Audio Power System		
Pt-1: Power Amp Board	502-01	£4.19
Spectrum DAC/ADC Board	502-02	£3.69
MARCH '85		
Modular Audio Power System		
Pt-2: Pre-Amp/Line Driver	503-01	£5.00
Main Board	503-02	£5.12
Heart Beat Monitor		
Detector	503-03	£8.90
Main Circuit Board	503-04	£6.62
Low Cost Speech Synthesiser	503-05	£3.42
APRIL '85		
Power Control Interface	504-01	£3.36
Disc Drive PSU	504-02	£6.54
Modular Audio Power System		
Pt-3: Test Signal Source	504-09	£4.20
Power Supply	504-10	£4.17
MAY '85		
Amstrad Synthesiser Interface	505-01	£4.23
Rugby Clock Pt-2	504-03	£24.22
"	504-04	£9.06
"	504-05	£5.12
"	504-06	£9.54
"	504-07	£5.40
"	504-08	£10.24