

PRACTICAL

APRIL 1987 · £1.25

# ELECTRONICS


SCIENCE & TECHNOLOGY

**PE VIGILANTE  
CAR ALARM**

**PE 30+30  
STEREO AMP**

**SWITCH MODE  
POWER SUPPLIES**

**INDUCTIVE LOOP  
REMOTE CONTROL**

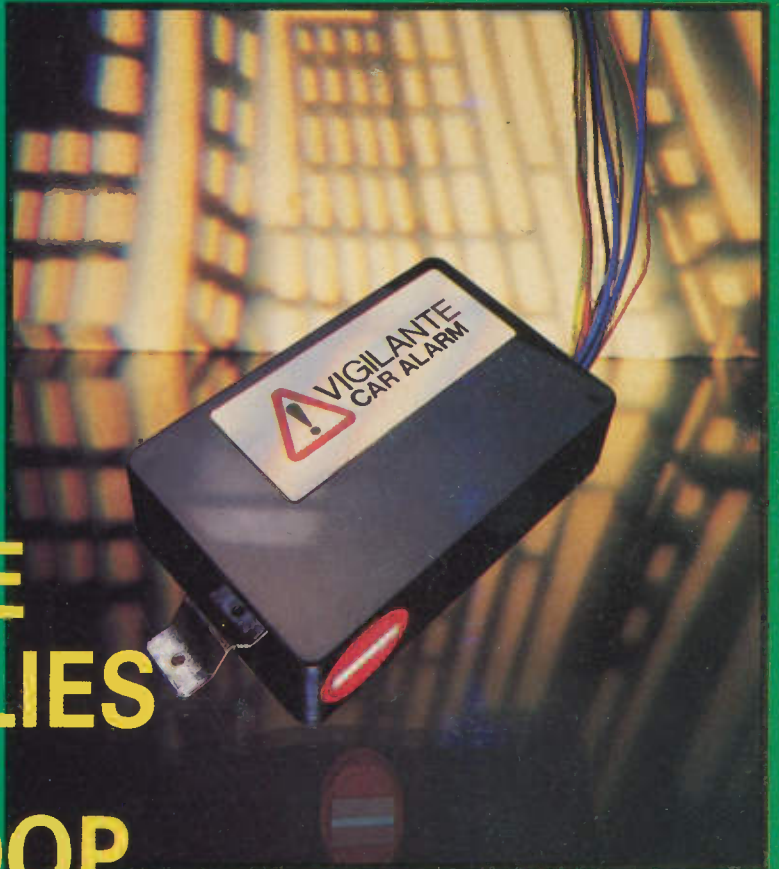

**DESIGN** – DC MOTORS  
TYPES AND FEATURES OF COMMON MOTORS

**COMPUTING** – DUAL OPTION  
EPROM PROGRAMMER FOR THE AMSTRAD

**TECHNOLOGY** – SENSORS  
ESSENTIAL INTERFACE DEVICES EXPLAINED

**EXPERIMENTAL ELECTRONICS**  
AND PRACTICAL APPLICATIONS – ALL IN THIS ISSUE

**PLUS:**

- ★ SPACEWATCH
- ★ LEADING EDGE
- ★ INDUSTRY NEWS
- ★ CIRCUIT IDEAS
- ★ LOGIC PUZZLE

THE SCIENCE MAGAZINE FOR SERIOUS ELECTRONICS AND COMPUTER ENTHUSIASTS

## CONSTRUCTIONAL PROJECTS


- PE VIGILANTE CAR ALARM** by Mike Delaney ..... 20  
 Keep your car alert to intruders – build a box to fox them!
- SWITCH MODE POWER SUPPLIES** by Robert Penfold ..... 34  
 Three practical circuits illustrating the principles discussed in the SMPSU Design feature.
- EXPERIMENTAL ELECTRONICS** by the Prof ..... 12  
 Inductive Loops. Ring the changes for your mobiles – remote control them via a cable loop.
- THE PE 30 PLUS 30 PART THREE** by Graham Nalty ..... 48  
 Concluding this high quality stereo amplifier design.

## SPECIAL FEATURES


- DESIGN – SMPSUS** by Robert Penfold ..... 26  
 Familiarity with subject names does not mean that they are understood. This article clarifies one such area – Switch Mode Power Supplies.
- TECHNOLOGY – SENSORS** by the Prof. .... 40  
 For data to be acted upon, it must first be detected. Sensors are a vital link in many control and measurement applications.
- DC MOTORS** by Brian Brooks ..... 52  
 During their history, direct current motors have been built and applied in countless different ways. Part two of this feature looks at more of them.

## REGULAR FEATURES


- MICROFORUM** by Stephen Burkitt ..... 44  
 The Amstrad is ideally suited to Eprom programming control. Here is a choice of two hardware interfaces.
- NEWS AND MARKET PLACE** ..... 4  
 News, views and new products from the world of electronics, plus countdown, catalogue casebook, firm contact and chipcount.
- PCB SERVICE** – professional PCBs for PE Projects ..... 60
- TRACK CENTRE** – the PCB track layout pages ..... 32
- BAZAAR** – readers' Have and Have-not marketplace ..... 62
- BINARY CHOP** – a powerful mental logic tester ..... 33
- SPACE WATCH AND THE SKY THIS MONTH**  
 by Dr. Patrick Moore OBE ..... 46
- THE LEADING EDGE** by Barry Fox ..... 8
- INDUSTRY NOTEBOOK** by Tom Ivall ..... 57

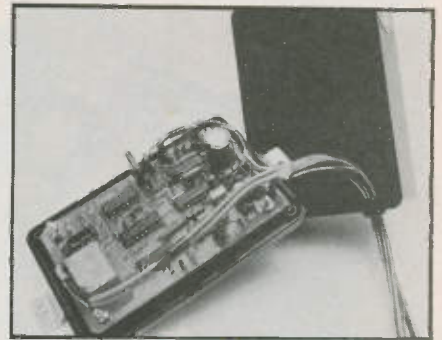


page 20

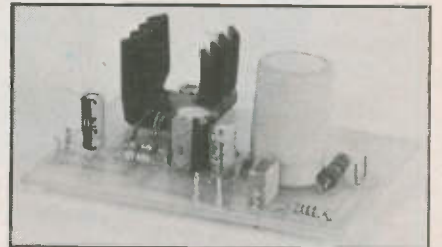

page 34

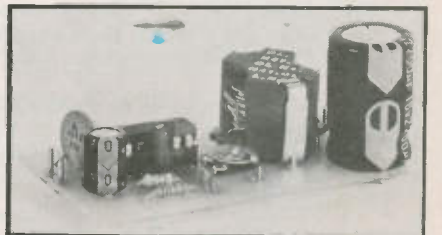

page 12

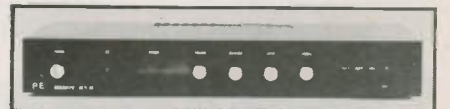

page 48



page 46



THE SCIENCE MAGAZINE FOR SERIOUS ELECTRONICS ENTHUSIASTS

# AMSTRAD EPROM PROGRAMMERS

STEPHEN BURKITT

*Simple design, inexpensive parts*


*The Amstrad's versatile sideways ROM is ideal for interfacing to an Eprom programmer. The I/O port can be used as an alternative.*

## CIRCUIT 1

THE AMSTRAD has a versatile sideways ROM ability yet the availability of Eprom programmers has been virtually nil. One or two are now appearing on the market, but are still extremely expensive. I therefore set out to build an inexpensive unit which would cater for the majority of Eproms, yet remain very simple and use only commonly available items. In fact, the whole prototype was built from surplus chips from my junk box.

The circuit is simple, requiring only an external variable power supply for the programming voltage. This can be easily constructed using the common single chip regulators. Fig.1. shows the wiring of the unit. The prototype was built on Vero V-Q prototype board, but any suitable type will do. The main part of the circuit revolves around the INTEL 8255 peripheral chip. This is a versatile circuit which can be programmed to almost any configuration to suit. The main use requires the chip to be in mode

0 which gives three eight bit ports, with port A, O/P, (low address), port C, O/P, (high address), and port B, data (set to input for verify and output for program). This is done by setting the control register (&80 for output and &82 for input). Bits 6,7 of port C are used as the chip select and program pulse respectively. In order to allow for different Eproms a customised jumper is used. A 14 pin header plug is suitable for this. The program supplied gives details of connections for various

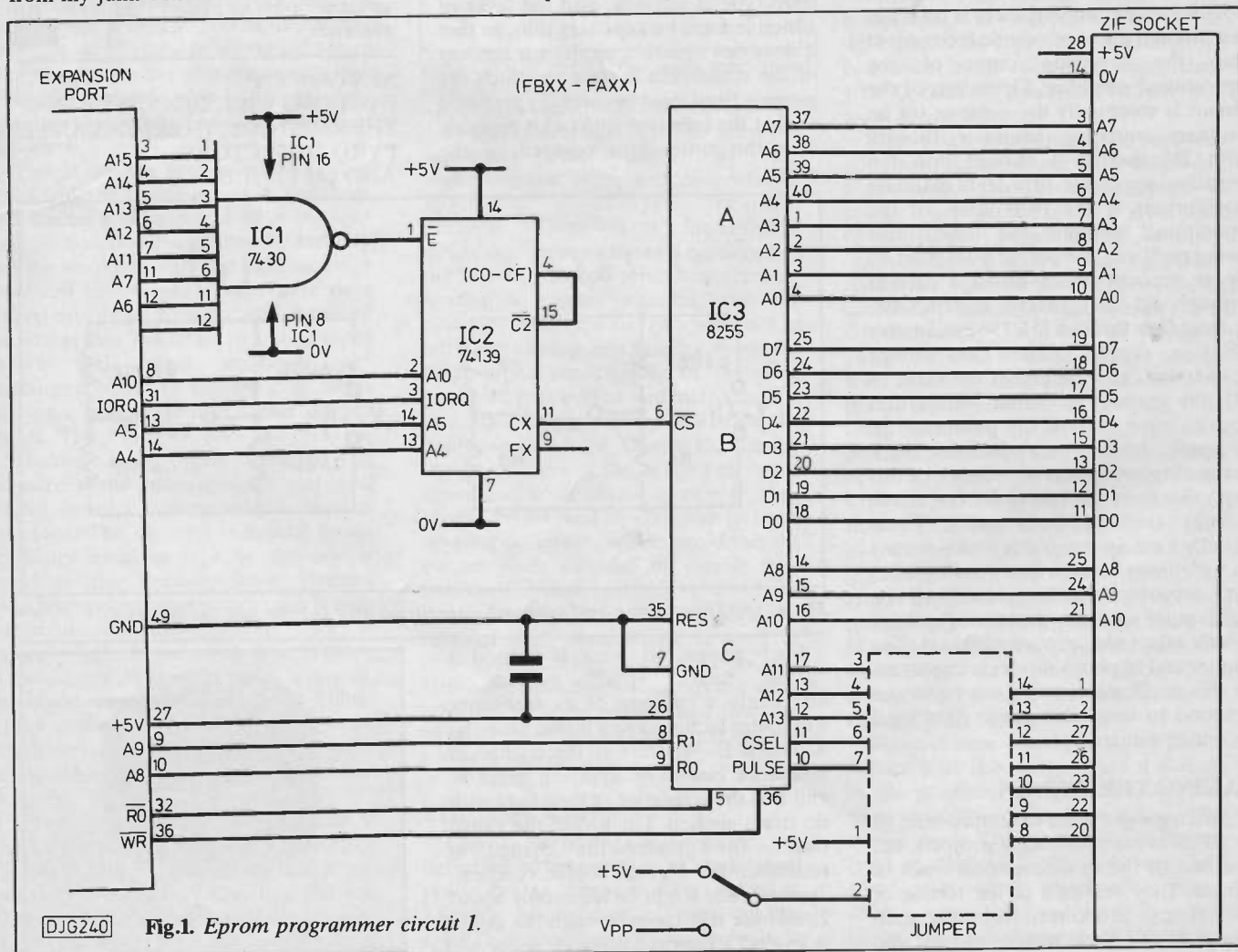

DJG240 Fig.1. Eprom programmer circuit 1.


Eproms. Address decoding is simple but conforms to the Amstrad specification. IC1 and IC2 give an I/O port base address of &F8E0. Use of a ZIF socket is recommended, but by no means essential. No protection is incorporated for incorrect insertion of Eproms so care must be taken in use.

**CIRCUIT 2**

The Amstrad I/O port (PE March 86) provides the Amstrad machines with a versatile port facility. One use of this would be as an Eprom programmer which can easily be achieved with just a few extra components. Along with a sideways ROM circuit board, this will

voltage regulator chips. A d.i.l. header is used to configure the p.c.b. for different Eproms. This may be left out if only one type will be used. Wiring for the jumper is displayed on the screen guide.

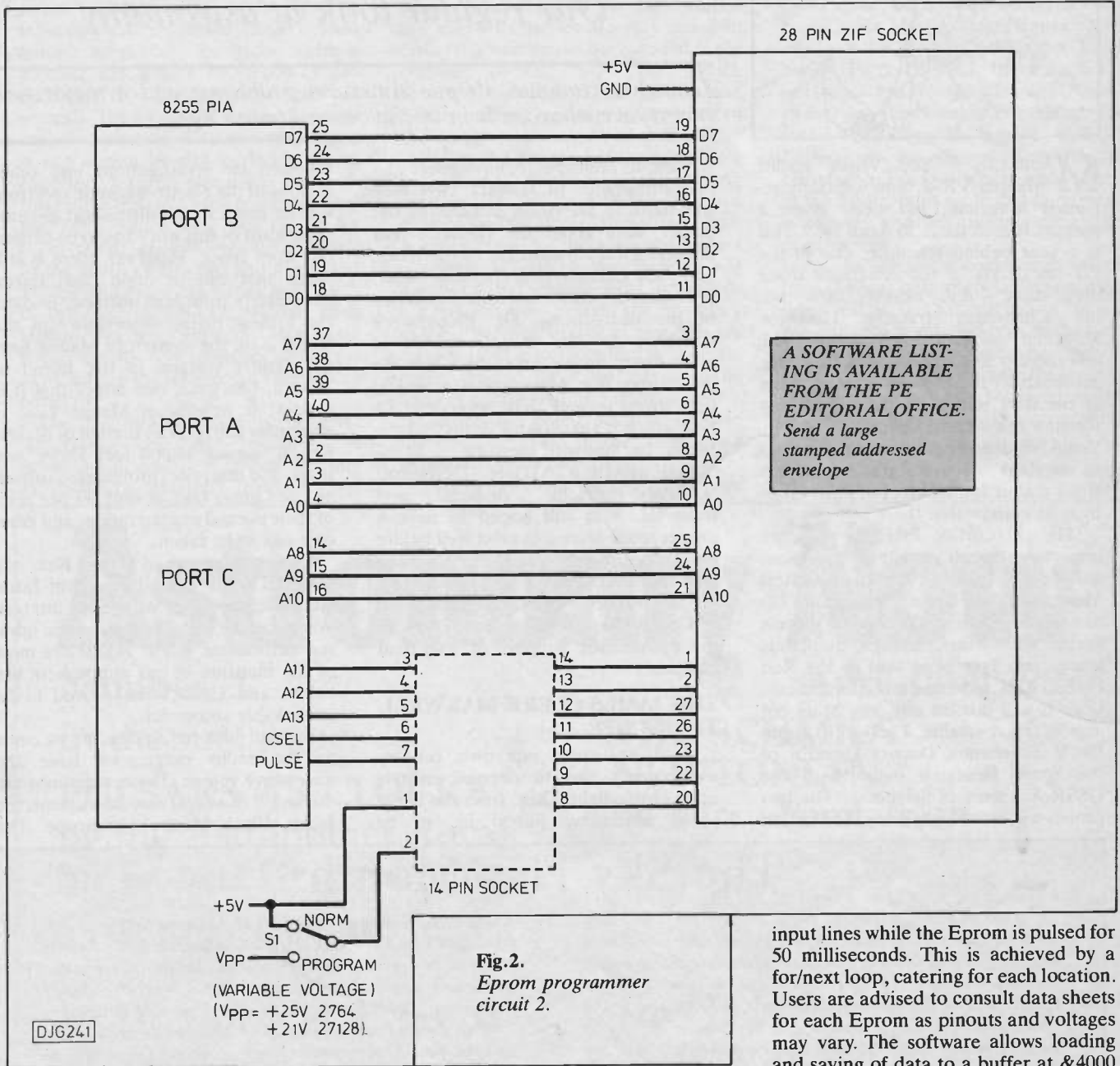Programming consists of setting the required address and data on the Eprom



Construction is straight forward. Sockets are best used for all i.c.s., and decoupling capacitors fitted. The unit should be checked for shorts following assembly, and it is advisable to check voltages with the p.c.b. connected before finally fitting the i.c.s.

In order to allow for flexibility in development the software was written in Basic. Instructions on use are provided in the program. A buffer starting at 16384 (&4000) is used for the Eprom data, and is the default setting. A screen dump facility exists which can also be directed to a printer if required.

enable the avid programmer to transfer programs onto ROM for instant use. The Amstrad firmware manuals give details of ROM code layout.

Fig. 2. gives details of a suitable addition to enable programming of Eproms from the basic 2716 to the 27128. The 27256 could be used with minor adaption. Software written in Basic was used as speed was not essential. The modular layout will enable easy translation to assembler code if required. An external low current variable power supply is required, and can easily be made using standard

input lines while the Eprom is pulsed for 50 milliseconds. This is achieved by a for/next loop, catering for each location. Users are advised to consult data sheets for each Eprom as pinouts and voltages may vary. The software allows loading and saving of data to a buffer at &4000 (16384), with printout to screen or printer as required. Locations may be set individually or in block. Bytes not required for programming must be set to &ff (255) if they are in the middle of the programming block. Eproms may only be erased by ultra-violet light.

The listing is adequately REM'ed for information on each module and on screen guidance is provided. Entry of addresses is in decimal, with confirmation in hexadecimal. Pressing Return will normally give default addresses of &4000 to &4000+ Eprom size.

PE