

EVERYDAY

MAY 1990

ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY


£1.40

**AMSTRAD SPEECH
SYNTHESISER**

QUIZMASTER

**ELECTRONIC
BAROMETER**


FREE INSIDE!

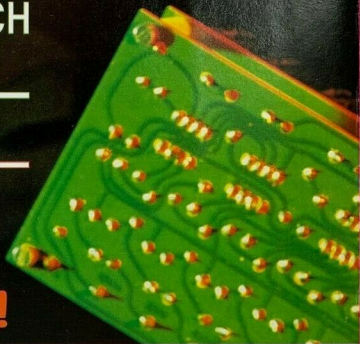

**SPECIAL
AMATEUR RADIO
SUPPLEMENT**

**SHORT WAVE
RECEIVER**

DIY AERIALS

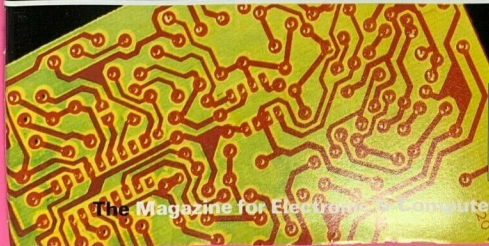




ISSN 0262-3617



9 770262 361003

The Magazine for Electronic & Computer Projects

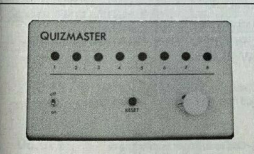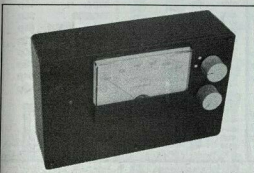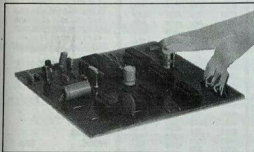ISBN 0262-3617
PROJECTS ... THEORY ... NEWS ...
COMMENT ... POPULAR FEATURES ...



Cover photograph by Reflections of Bournemouth

© Wimborne Publishing Ltd 1990. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduced or imitations in whole or in part are expressly forbidden.

Projects

- AMSTRAD CPC SPEECH SYNTHESISER** by Robert Penfold **304**
If only your Amstrad could talk!
- ELECTRONIC BAROMETER** by Owen Bishop **310**
Take some of the guesswork out of local "weather forecasting"
- AZIMUTH ADJUSTMENT AID** by T. R. de Vaux-Balbirnie **322**
You don't have to scrap your old tape recorder — bring it back to life!
- S. W. RADIO** by Robert Penfold **Supp-7**
"Tweak" and "Twiddle" your way around the world
- QUIZMASTER** by Adrian Galea **328**
A question of logic
- AUTO MEMO** by Owen Bishop **342**
Get your message across loud and clear

Series

- MICRO IN CONTROL — PART 6** by John Hughes **316**
Counting circuits and control logic
- ROBOT ROUNDUP** by Nigel Clark **326**
Investigating the world of robots
- ON SPEC** by Mike Tooley **334**
The place for Spectrum and Sam miro owners
- ACTUALLY DOING IT** by Robert Penfold **346**
Considering mains power
- AMATEUR RADIO** by Tony Smith G4FA1 **348**
Mouse Decoders and Keyboards; Alternative Test
- BBC MICRO** by Robert Penfold **350**
Communications applications

Features

- EDITORIAL** **303**
- SHOPTALK** by David Barrington **319**
Product news and component buying
- FOR YOUR ENTERTAINMENT** by Barry Fox **320**
Hot Tip; Lap-Top Rambo; DATs Music
- MARKET PLACE** **333**
Free readers buy, sell and swap spot
- POWER SUPPLIES FOR PROJECTS** by Vivian Capel **336**
Pitfalls to look out for when designing mains power supplies
- DOWN TO EARTH** by George Short **340**
Valves past and future
- DIRECT BOOK SERVICE** **352**
Selected technical books by mail order
- PRINTED CIRCUIT BOARD SERVICE** **356**
- ADVERTISERS INDEX** **360**

FREE

between pages 326 and 327

AMATEUR RADIO SUPPLEMENT (12-pages)
Shortwave Reception — Crystal Set — DIY Aerials — T.R.F. Receiver

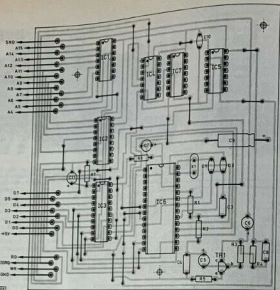


Fig. 3 (above) Printed circuit board component layout and wiring details. (below) Full size printed circuit copper foil master pattern

The second complication is that we require separate outputs for read and write operations. This is achieved by gating the output of IC2 with the RD (read) and WR (write) lines of the CPC expansion bus, using a separate OR gate for each of these two lines. This gives a negative read pulse from IC4b, and a negative write pulse from IC4a.

A positive pulse is needed for the ALD input of the speech chip, and this is derived from the write output by inverter IC7. The six bit latching output for IC3 is provided by IC3, which is actually an octal D type flip-flop. In this case only six of the just being ignored. IC4a provides a negative pulse to the "clock pulse" input of IC3 during write operations to the interface, and this latches the outputs of the flip-flops.

At switch-on a negative reset pulse is supplied to IC2 by C11. This ensures that IC3 commences with all its outputs low, and that the speech chip does not produce any output until the user activates it. RT ensures that C11 is rapidly discharged when the computer is switched off, so that a fresh reset pulse is produced when it is switched on again.


IC5 is a quad tri-state buffer, but in this circuit only one buffer is used and no connections are made to the other three. It buffers the LRO output of IC5 to drive the CPC expansion bus, and is set to be active state by the output pulses from IC4 during read operations to the speech synthesiser.

Power for the speech synthesiser is obtained from the +5 volt supply output of the CPC expansion port. C9 provides smoothing which helps to give a low noise level on the audio output of the unit.

CONSTRUCTION

Details of the printed circuit board are provided in Fig. 1. Crystal X1 must be a miniature wire-wound type with 0.2 inch

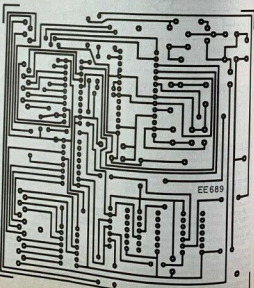lead spacing if it is to fit easily into the board. Try to complete the soldered joints reasonably rapidly when lifting this component as some crystals are sensitive to



Completed circuit board showing all the i.c.s. mounted in i.c. holders.

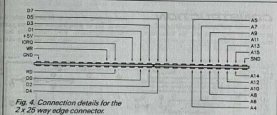


Fig. 4. Connection details for the 25-way edge connector.

damaged by heat. IC5 is a MOS integrated circuit, and as such it is vulnerable to damage by static charges.

Leave this component in its anti-static packaging until, in all other respects, the unit is finished. Then fit this component onto the board, handling it as little as possible, avoiding touching the pins and fitting it into a holder already fitted to the board so that there is no need to make any direct soldered connections to this chip.

With a fairly large integrated circuit of this type, IC5 can be a bit difficult to fit into its socket. Usually the pins have to be carefully bent inwards slightly. Be careful not to buckle any of its pins when fitting it into its socket. Although none of the other integrated circuits are static sensitive types, it is recommended that they should be fitted in holders.

There should be no difficulties in fitting the other components onto the board, provided the correct types of capacitor are used. In particular, the polyester types should have a lead spacing of 7.5 millimetres (0.3 inches). Be careful to fit the electrolytic capacitors with the cor-

rect polarity. A number of link wires are required, and these can be made from 22 s.w.g. tinned copper wire, or the leads trimmed from the resistors and capacitors which will be sufficient.

CONNECTIONS

The board is connected to the computer via a 25-way ribbon cable which is fitted with a 2 by 25-way 0.1 inch pitch edge connector at the computer end. At the other end it is either connected directly to the board, or via pins if preferred.

Both ends of the cable should be prepared by separating all the wires, stripping a few millimetres of insulation from each one, and tinning them all with solder. The terminals of the edge connector (or the twenty five that are used anyway) should be tinned with solder, as should the pins on the board if this method of connection is adopted.

In my experience the CPC computers are not tolerant of long connecting leads on their expansion bus. It is therefore recommended that the connecting cable should be no more than about 6 metres long.

The edge connector connection details are given in Fig. 4. The board has been designed so that the order of the connections on the board matches up well with that of those on the edge connector. There is no need for any crossing over of wires, but you will need to be very careful to get each lead connected to the right terminal of the edge connector.

The multi-coloured "rainbow" ribbon cable is better for this sort of thing, but any ribbon cable is usable if you take extra care. If you are using a connector fitted with the appropriate polarising key, make quite sure that you orient the connector the right way up before making the connections to it.

If the connector is not fitted with a polarising key, clearly mark the top and bottom edges such as to minimise the risk of fitting it to the expansion port upside-down. Once this wiring has been completed, check it very thoroughly at least once before connecting the unit to the computer and trying it out.

Projects of this type are often left as untested boards, as was the prototype. However, it should not be difficult to fit the unit into a small plastic case if preferred. This does have the advantages of being a bit neater, and keeping dust etc. off the circuit board.

COMPONENTS

Resistors

- R1, R2 27k (2 off)
- R3 1M
- R4 4.7k
- R5 4.7k
- R6, R7 10k (2 off)

All 0.25W 5% carbon

Capacitors

- C1 120 ceramic plate
- C2 100 ceramic plate
- C3 22n polyester (7.5mm pitch)
- C4, C8 10n polyester (7.5mm pitch) (2 off)
- C5 1µ radial elect. 63V
- C6 2µ radial elect. 63V
- C7, C11 220µ radial elect. 10V (2 off)
- C8 330µ axial elect. 10V
- C10 100n disc ceramic

Semiconductors

- IC1 74LS138 3-to-8 line NAND gate decoder
- IC2 74LS273 octal flip-flop
- IC3 74LS32 quad 2-input OR gate
- IC4 74LS32 quad 2-input OR gate
- IC5 74LS125 quad tri-state buffer
- IC6 SN7526 speech synthesiser
- IC7 74LS14 5 inverters
- TR1 BC549 silicon npn

Miscellaneous

- X1 3.2768MHz miniature wire-wound crystal (see text)

Printed circuit board available from the *EE PCB Service*, order code EE685; cases (see text) £ 2.00; 25-way ribbon cable, edge connector, 25-way ribbon cable, 14 pin D.I.L. holder (4 off); 16 pin D.I.L. holder; 20 pin D.I.L. holder; 28 pin D.I.L. holder; connecting wire, etc.

Approx cost Guidance only

£20